
Transistors and Amplification

Introduction to Transistors (BJT and FET)

A **transistor** is one of the most important components in electronics. It acts as a **switch** or an **amplifier** in a circuit. Transistors are used in almost every electronic device — from radios and computers to smartphones.


There are two main types of transistors:

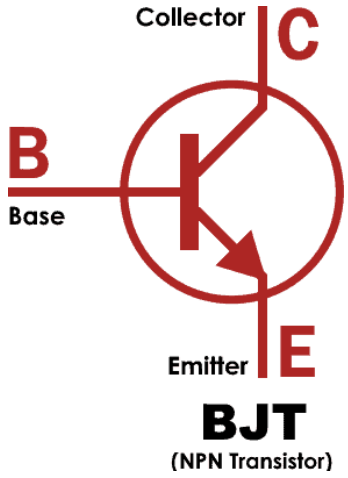- **BJT (Bipolar Junction Transistor)** – It uses both **electrons and holes** to conduct current. It has three parts: **Emitter, Base, and Collector**.





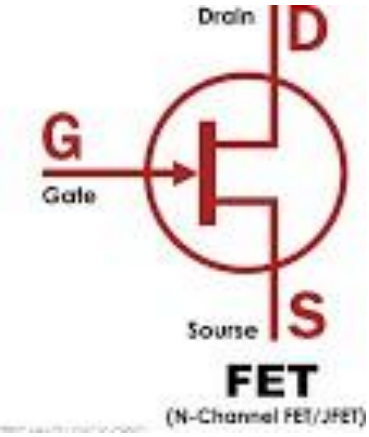- **FET (Field-Effect Transistor)** – It uses **electric fields** to control current flow. It also has three parts: **Source, Gate, and Drain**.\






Both BJTs and FETs control large currents using small input signals, making them essential for signal processing and control in circuits.


Transistor Operation (Switching and Amplification)

A transistor works in two main ways: **as a switch** and **as an amplifier**.

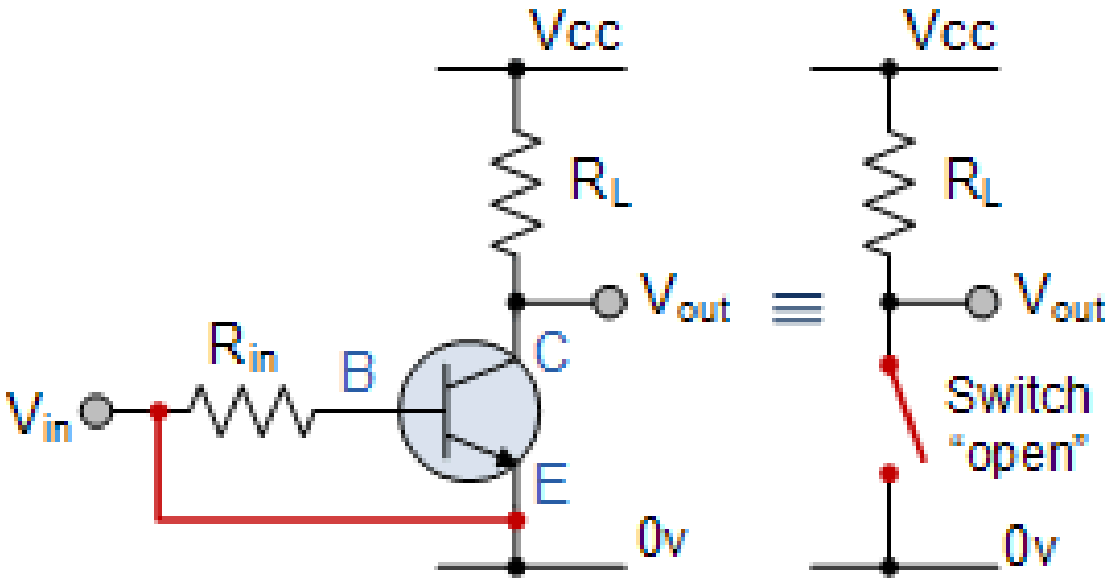- **As a Switch:**
  When used as a switch, the transistor turns current **on or off**. If a small current flows into the base (for BJT) or gate (for FET), it allows a larger current to flow between the other two terminals. This principle is used in **digital electronics**, such as computers, logic gates, and microcontrollers.



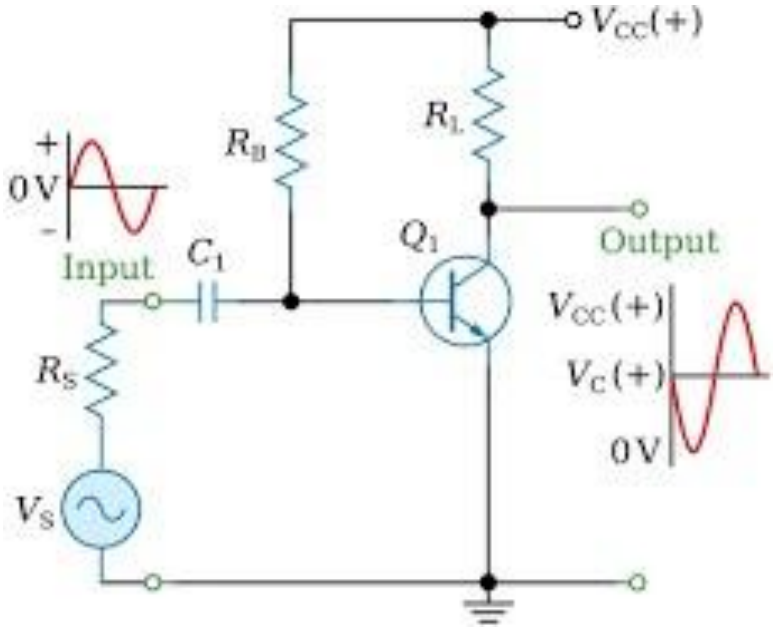- **As an Amplifier:**
  When used as an amplifier, the transistor **increases the strength of a signal**. A small input signal at the base or gate controls a larger output current at the collector or drain. This is how transistors make weak audio or radio signals stronger — they're key parts of **amplifiers, speakers, and radios**.



Basic Transistor Circuits (Switch and Amplifier)

1. **Transistor Switch Circuit**
    - The transistor is “OFF” when there is no base current.
    - When a small base current is applied, it turns “ON” and allows a larger current to flow from collector to emitter.
    - Example: Used in LED blinking circuits or relays.
2. **Transistor Amplifier Circuit**
    - A weak input signal enters the base of the transistor.
    - The transistor boosts this signal and outputs a stronger version at the collector.
    - Example: Used in microphone or speaker circuits.

Applications in Circuits

Transistors are used in many electronic applications, including:

- **Switching circuits** in computers and microcontrollers

- **Audio amplifiers** in speakers and radios
- **Signal processing** in communication systems
- **Voltage regulation** and **power control** circuits

Essentially, transistors are like the “brain cells” of electronics — they help control, switch, and amplify electrical signals in almost every device.

A **transistor** is a small but powerful device that can **control, switch, and amplify** electrical signals — making it one of the building blocks of modern electronics.

References:

https://byjus.com/physics/bipolar-junction-transistor/
https://www.electronics-tutorials.ws/transistor/tran_1.html